

B.Sc. DEGREE EXAMINATION, APRIL 2020
I Year I Semester
Digital Logic Fundamentals

Time : 3 Hours

Max.marks :75

Section A ($10 \times 2 = 20$) Marks

Answer any **TEN** questions

1. Draw the symbols of Universal gates.
2. What is PLA?
3. What is the purpose of Decoder?
4. Draw the logic diagram of RS flipflop.
5. Give two examples for complement numbers
6. Convert $(127.85)_{10}$ to $()_2$
7. Draw the truth tables for 3 input OR Gate
8. Convert 1101.11 to decimal equivalent.
9. Draw the logic diagram of D-flipflop.
10. What is the purpose of shift register?
11. List down the different types of RAM.
12. What is Up down counter?

Section B ($5 \times 5 = 25$) Marks

Answer any **FIVE** questions

13. Describe about Karnaugh map with example.
14. Write about parity generators in detail.
15. Explain about shift registers and its types.
16. What is BCD ripple counter? Draw its logic diagram.
17. Draw the truth tables for all the flip flops
18. Briefly explain about memory addressing.
19. Explain about full adder with examples.

Section C ($3 \times 10 = 30$) Marks

Answer any **THREE** questions

20. Convert any decimal into a number of base 3, base 4, base 7 and base 16.
21. Explain about BCD adder in detail.
22. Explain about multiplexer with neat diagram
23. Explain about the Master Slave flip flops.
24. Explain about ROM in detail.

B.Sc. DEGREE EXAMINATION, APRIL 2020
I Year I Semester
Digital Logic Fundamentals

Time : 3 Hours

Max.marks :75

Section A ($10 \times 2 = 20$) Marks

Answer any **TEN** questions

1. Draw the symbols of Universal gates.
2. What is PLA?
3. What is the purpose of Decoder?
4. Draw the logic diagram of RS flipflop.
5. Give two examples for complement numbers
6. Convert $(127.85)_{10}$ to $()_2$
7. Draw the truth tables for 3 input OR Gate
8. Convert 1101.11 to decimal equivalent.
9. Draw the logic diagram of D-flipflop.
10. What is the purpose of shift register?
11. List down the different types of RAM.
12. What is Up down counter?

Section B ($5 \times 5 = 25$) Marks

Answer any **FIVE** questions

13. Describe about Karnaugh map with example.
14. Write about parity generators in detail.
15. Explain about shift registers and its types.
16. What is BCD ripple counter? Draw its logic diagram.
17. Draw the truth tables for all the flip flops
18. Briefly explain about memory addressing.
19. Explain about full adder with examples.

Section C ($3 \times 10 = 30$) Marks

Answer any **THREE** questions

20. Convert any decimal into a number of base 3, base 4, base 7 and base 16.
21. Explain about BCD adder in detail.
22. Explain about multiplexer with neat diagram
23. Explain about the Master Slave flip flops.
24. Explain about ROM in detail.