

SHRIMATHI DEVKUNVAR NANALAL BHATT VAISHNAV COLLEGE FOR WOMEN  
(AUTONOMOUS)

(Affiliated to the University of Madras and Re-accredited with 'A+' Grade by NAAC)  
Chromepet, Chennai — 600 044.

B.Sc.(Physics) - END SEMESTER EXAMINATIONS APRIL-2023

SEMESTER - VI

**20UPHCT6014 - Integrated Electronics**

Total Duration : 2 Hrs 30 Mins.

Total Marks : 60

### Section B

Answer any **SIX** questions ( $6 \times 5 = 30$  Marks)

1. Show that NAND gate is a universal gate.
2. What is a full adder? Illustrate how a full adder can be constructed using half adders.
3. Construct a D flip flop and explain its working.
4. Examine the working of Non-inverting summing amplifier.
5. Outline how a Schmitt trigger can be constructed using 555 timer.
6. Sketch a MOD 16 counter, with a proper working table and output waveform.
7. Construct a Wien Bridge Oscillator and discuss its working.
8. With necessary block diagram, explain the working of the A/D converter by successive approximation method.

### Section C

Answer any **THREE** questions ( $3 \times 10 = 30$  Marks)

9. Explain the K map method of solving expressions.
10. Illustrate the working of a multiplexer in detail and give its uses.
11. Construct and discuss the working of shift registers. Enlist its application.
12. Outline the working of an Op-Amp as a differentiator. Explain the response of the differentiator for various wave inputs.
13. Construct a binary weighted resistor D/A converter.

\*\*\*\*\*